

1 Introduction

The goal of this lab is to use Laplace transforms to find the time-domain response of an RLC bandpass filter to impulse and step inputs.

2 Equations

We used the transfer function from pre-lab to find the Impulse response and the step response.

$$H(s) = \frac{v_{out}(s)}{v_{in}(s)} = \frac{\frac{s}{cR}}{s^2 + \frac{s}{cR} + \frac{1}{cL}} \quad (1)$$

$$y(t) = \frac{|g|}{w} e^{at} \sin(wt + \angle g) u(t) \quad (2)$$

$$H(t) = (5000 + j1344.08)e^{(-5000t + j18.6 \cdot 10^3 t)} + (5000 - j1344.08)e^{(-5000t - j18.6 \cdot 10^3 t)} \quad (3)$$

$$\text{Final - value - of - step - response} = \lim_{s \rightarrow 0} sH(s)u(s) = \lim_{s \rightarrow 0} H(s) = \lim_{s \rightarrow 0} \frac{\frac{s}{cR}}{s^2 + \frac{s}{cR} + \frac{1}{cL}} = 0 \quad (4)$$

3 Methodology and Results


This lab consists of two parts:

- Part 1:

In this part, we started with finding the impulse response $h(t)$ that we found by hand in the prelab assignment:

```
1      ### part 1 task 1
2
3      steps = 1e-5
4      t = np.arange(0, 1.2e-3 + steps, steps)
5
6      def h(t):
7          h = (5000+1345j)*np.exp(-(5000+18584j)*t)+(5000-1345j)*np.exp
      ((-5000-18584j)*t)
8          return h
9      plt.figure(figsize=(10,7))
10     plt.subplot(1, 1, 1)
11     plt.plot(t,h(t))
12     plt.grid()
13     plt.ylabel ('h(t)')
14     plt.xlabel('t [s]')
15     plt.title ('Impulse Response by hand')
16
17
```


The output of this is:

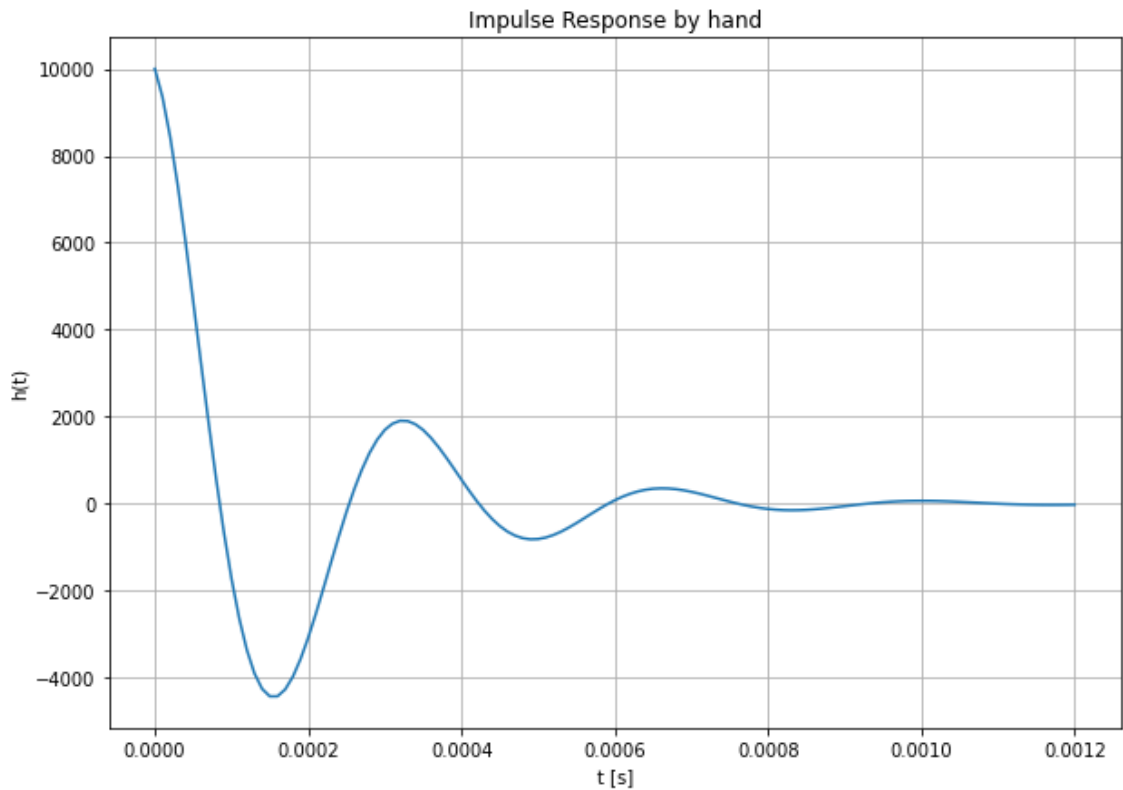

Then We were asked to do the impulse response function using `scipy.signal.impulse()` as in the following:

```
1      ### part 1 task 2
2
3      R = 1000
4      L = 27e-3
5      c = 100e-9
6
7      num = [0 , 1/(R*c) , 0]
8      den = [1 , 1/(c*R) , 1/(c*L)]
9
10     tout , yout = sig.impulse(( num , den ) , T = t )
11
12     plt.figure(figsize=(10,7))
13     plt.subplot(1, 1, 1)
14     plt.plot(tout, yout)
15     plt.grid()
16     plt.ylabel ('h(t)')
17     plt.xlabel('t [s]')
18     plt.title ('Impulse Response')
19
```

The output of this is:

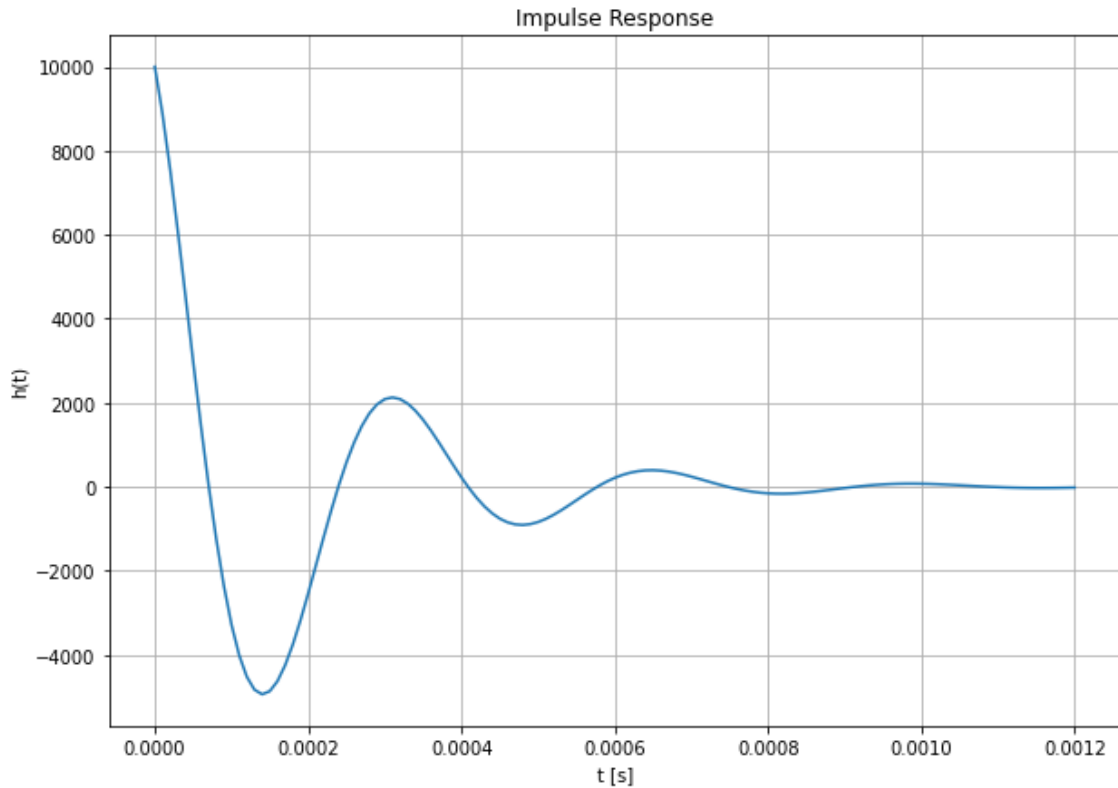

- Part 3:


In this part, we find the step response of $H(s)$ using the `scipy.signal.step()` function:

```

1      ### part 2 task 1
2
3      num = [0 , 1/(R*c) , 0]
4      den = [1 , 1/(c*R) , 1/(c*L)]
5
6      tout , yout = sig.step(( num , den ) , T = t )
7
8      plt.figure(figsize=(10,7))
9      plt.subplot(1, 1, 1)
10     plt.plot(tout, yout)
11     plt.grid()
12     plt.ylabel ('y(t)')
13     plt.xlabel('t [s]')
14     plt.title ('Step Response')
15     plt.show()
16
17

```

The output is:

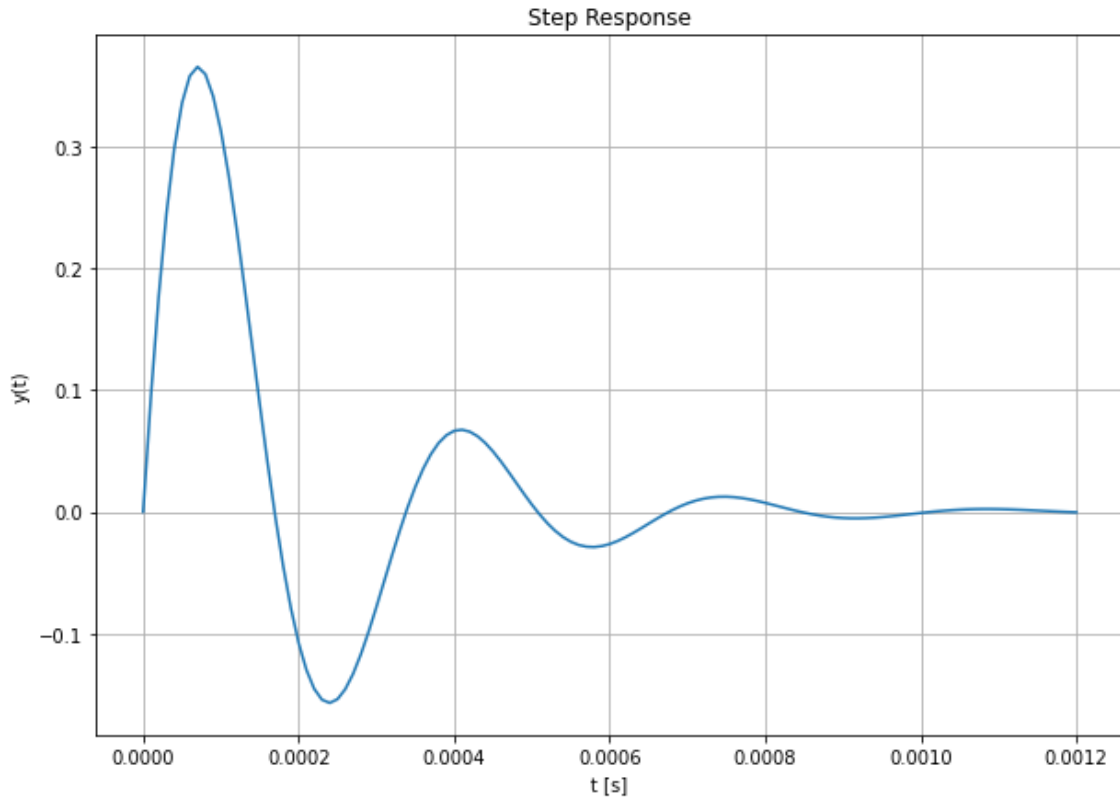

The result of this part is different than part one. This part starts at 0 when $t=0$ where part 1 starts at 10000. Also, the maximum value of each part is different.

4 Questions

1. Explain the result of the Final Value Theorem from Part 2 Task 2 in terms of the physical circuit components.

After a long enough time the capacitor will be open circuit and the inductor will be a short circuit that is why the voltage will be zero at the output.

2. Leave any feedback on the clarity of the expectations, instructions, and deliverables.

5 Conclusion

At the end of this lab, we become familiar on how use Laplace transforms to find the time-domain response of an RLC bandpass filter to impulse and step inputs.